



CS302P
LAB QUIZZES
FINAL TERM
FALL 2024
BY
BUTTERCUP
FOR LMS HANDLING
CONTACT
0324-9427076
THE BRAINY SQUAD

**CS302P - Digital Logic Design (Practical) (Attendance Quiz # 9 - (Not Graded))****Question # 5 of 5 (Start time: 11:06:49 PM, 10 January 2025)**

The parallel outputs of a counter circuit represent the _____

Select the correct option

<input type="radio"/>	Parallel data word
<input checked="" type="radio"/>	Counter modulus
<input type="radio"/>	Clock count
<input type="radio"/>	Clock frequency

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 9 - (Not Graded))

Question # 4 of 5 (Start time: 11:06:22 PM, 10 January 2025)

Which of the following is the modified code of Excess-3 code?

Select the correct option

<input checked="" type="radio"/>	Gray Code
<input type="radio"/>	EBDIC
<input type="radio"/>	BCD
<input type="radio"/>	ASCII



Graded))

Question # 3 of 5 (**Start time: 11:06:03 PM, 10 January 2025**)

A circuit that compares two numbers and determines their magnitude is called _

Select the correct option



Size comparator



Magnitude comparator



Inverter



Height comparator

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 9 - (Not Graded))

Question # 2 of 5 (Start time: 11:05:30 PM, 10 January 2025)

How many flop flops are required to create a counter circuit which can count from 0 to 7?

Select the correct option

- | | |
|----------------------------------|---|
| <input type="radio"/> | 2 |
| <input checked="" type="radio"/> | 3 |
| <input type="radio"/> | 1 |
| <input type="radio"/> | 4 |

BUTTERCUP
0324-9427076

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 9 - (Not Graded))

Question # 1 of 5 (Start time: 11:05:05 PM, 10 January 2025)

An identify comparator is defined as a digital comparator which has _____

Select the correct option

<input checked="" type="radio"/>	Only one output terminal
<input type="radio"/>	Two output terminals
<input type="radio"/>	Three output terminals
<input type="radio"/>	No output terminals



Question # 5 of 5 (**Start time: 10:46:44 PM, 10 January 2025**)

TTL 74LS85 is a _____

Select the correct option

<input type="radio"/>	8-bit magnitude comparator
<input type="radio"/>	8-bit word comparator
<input type="radio"/>	1-bit digital comparator
<input checked="" type="radio"/>	4-bit magnitude comparator

**Question # 2 of 5 (Start time: 10:45:44 PM, 10 January 2025)**

An identify comparator is defined as a digital comparator which has

Select the correct option

<input type="radio"/>	No output terminals
<input type="radio"/>	Three output terminals
<input checked="" type="radio"/>	Only one output terminal
<input type="radio"/>	Two output terminals



vulms.vu.edu.pk/



Graded))

Question # 1 of 5 (Start time: 10:45:25 PM, 10 January 2025)

Comparators are used in _____

Select the correct option

<input type="radio"/>	Memory
<input type="radio"/>	Motherboard
<input type="radio"/>	Hard Drive
<input checked="" type="radio"/>	CPU



vulms.vu.edu.pk/()

Question # 9 of 10 (**Start time: 09:30:19 PM, 08 January 2025**)

TTL 74LS85 is a _____

Select the correct option



8-bit magnitude comparator



8-bit word comparator



4-bit magnitude comparator



1-bit digital comparator

CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)

Question # 8 of 10 (Start time: 09:29:07 PM, 08 January 2025)

The parallel outputs of a counter circuit represent the _____

Select the correct option

<input type="radio"/>	Parallel data word
<input type="radio"/>	Counter modulus
<input checked="" type="radio"/>	Clock count
<input type="radio"/>	Clock frequency

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)****Question # 6 of 10 (Start time: 09:28:20 PM, 08 January 2025)**

Which one is a basic comparator?

Select the correct option

<input type="radio"/>	OR
<input type="radio"/>	NAND
<input checked="" type="radio"/>	XOR
<input type="radio"/>	AND

CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)

Question # 5 of 10 (**Start time: 09:27:45 PM, 08 January 2025**)

Three decade counter would have _____

Select the correct option

<input type="radio"/>	2 BCD counters
<input checked="" type="radio"/>	3 BCD counters
<input type="radio"/>	5 BCD counters
<input type="radio"/>	4 BCD counters

CS302P – Digital Logic Design (Practical) (Semester Quiz # 04)

Question # 4 of 10 (**Start time: 09:27:08 PM, 08 January 2025**)

Convert the Gray code 1011 to binary.

Select the correct option

<input checked="" type="radio"/>	1101
<input type="radio"/>	0111
<input type="radio"/>	1011
<input type="radio"/>	1010

BUTTERCUP
0324-9427076

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)****Question # 2 of 10 (Start time: 09:26:16 PM, 08 January 2025)**

Reflected Binary Code is also known as _____ code.

Select the correct option

<input type="radio"/>	BCD
<input type="radio"/>	ASCII
<input checked="" type="radio"/>	Gray Code
<input type="radio"/>	Excess-3

**Question # 1 of 10 (Start time: 09:25:41 PM, 08 January 2025)**

Which of the following is an invalid BCD code?

Select the correct option

<input type="radio"/>	1001
<input type="radio"/>	0011
<input checked="" type="radio"/>	1101
<input type="radio"/>	0101

8:32 PM

Vo WiFi 4G 80.7 K/S 42



vulms.vu.edu.pk/



CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)

Quiz

Question # 10 of 10 (Start time: 08:31:41 PM, 08 January 2025)

A counter circuit is usually constructed of _____

Select the correct option



A number of latches connected in cascade form



A number of NOR gates connected in cascade form



A number of NAND gates connected in cascade form



A number of flip-flops connected in cascade

BUTTERCUP
0324-9427076

Click to See

**Question # 9 of 10 (Start time: 08:31:34 PM, 08 January 2025)**

Comparators are used in _____

Select the correct option

<input type="radio"/>	Hard Drive
<input type="radio"/>	CPU
<input type="radio"/>	Motherboard
<input type="radio"/>	Memory



vulms.vu.edu.pk/

**Question # 8 of 10 (Start time: 08:30:10 PM, 08 January 2025)**

What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops?

Select the correct option Relo


- | | |
|----------------------------------|----------------|
| <input checked="" type="radio"/> | 0 to $2^n - 1$ |
| <input type="radio"/> | 0 to $2^n + 1$ |
| <input type="radio"/> | 0 to 2^n |
| <input type="radio"/> | 0 to 2^{n+1} |



Click to Save Answer & Move



vulms.vu.edu.pk/()

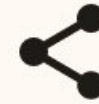

CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)

Quiz Start Time: 08:26 PM

Question # 8 of 10 (Start time: 08:30:10 PM, 08 January 2025)

What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops?

Select the correct option



- | | |
|----------------------------------|----------------|
| <input checked="" type="radio"/> | 0 to $2^n - 1$ |
| <input type="radio"/> | 0 to $2^n + 1$ |
| <input type="radio"/> | 0 to 2^n |
| <input type="radio"/> | 0 to 2^{n+1} |

CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)

Question # 7 of 10 (**Start time: 08:29:38 PM, 08 January 2025**)

An identify comparator is defined as a digital comparator which has _____

Select the correct option

<input type="radio"/>	No output terminals
<input type="radio"/>	Two output terminals
<input type="radio"/>	Three output terminals
<input checked="" type="radio"/>	Only one output terminal

**Question # 6 of 10 (Start time: 08:29:13 PM, 08 January 2025)**

Three decade counter would have _____

Select the correct option

<input type="radio"/>	2 BCD counters
<input checked="" type="radio"/>	3 BCD counters
<input type="radio"/>	5 BCD counters
<input type="radio"/>	4 BCD counters

Question # 5 of 10 (**Start time: 08:28:33 PM, 08 January 2025**)

A decimal counter has _____ states.

Select the correct option

<input type="radio"/>	2
<input checked="" type="radio"/>	10
<input type="radio"/>	9
<input type="radio"/>	7

CS302P – Digital Logic Design (Practical) (Semester Quiz # 04)

Question # 4 of 10 (Start time: 08:27:58 PM, 08 January 2025)

Ripple counters are also called _____

Select the correct option

<input type="radio"/>	VLSI counters
<input checked="" type="radio"/>	Asynchronous counters
<input type="radio"/>	Synchronous counters
<input type="radio"/>	SSI counters

BUTTERCUP
0324-9427076

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)****Question # 3 of 10 (Start time: 08:27:21 PM, 08 January 2025)**

Why do we use Gray Code?

Select the correct option

<input type="radio"/>	Invert the code
<input type="radio"/>	Error Detection
<input checked="" type="radio"/>	To count the number or bit changes
<input type="radio"/>	Error Correction

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)****Question # 2 of 10 (Start time: 08:26:37 PM, 08 January 2025)**

Which of the following is the modified code of Excess-3 code?

Select the correct option

<input checked="" type="radio"/>	BCD
<input type="radio"/>	Gray Code
<input type="radio"/>	ASCII
<input type="radio"/>	EBDIC

CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)

Question # 1 of 10 (**Start time: 08:26:05 PM, 08 January 2025**)

In a comparator, if we get input as $A > B$ then the output will be _____

Select the correct option

<input type="radio"/>	0
<input type="radio"/>	A
<input type="radio"/>	B
<input checked="" type="radio"/>	1

BUTTERCUP
0324-9427076

**Question # 10 of 10 (Start time: 07:28:07 PM, 08 January 2025)**

In a comparator, if we get input as $A > B$ then the output will be _____

Select the correct option

- | | |
|----------------------------------|---|
| <input type="radio"/> | A |
| <input type="radio"/> | 0 |
| <input checked="" type="radio"/> | 1 |
| <input type="radio"/> | B |

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)****Question # 9 of 10 (Start time: 07:27:34 PM, 08 January 2025)**

Which one is a basic comparator?

Select the correct option

<input type="radio"/>	OR
<input type="radio"/>	NAND
<input checked="" type="radio"/>	XOR
<input type="radio"/>	AND

**Question # 8 of 10 (Start time: 07:27:00 PM, 08 January 2025)**

Convert the Gray code 1011 to binary.

Select the correct option

<input checked="" type="radio"/>	1101
<input type="radio"/>	1010
<input type="radio"/>	1011
<input type="radio"/>	0111

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)****Question # 7 of 10 (Start time: 07:26:29 PM, 08 January 2025)**

A counter circuit is usually constructed of _____

Select the correct option

- | | |
|----------------------------------|--|
| <input type="radio"/> | A number of NOR gates connected in cascade form |
| <input type="radio"/> | A number of NAND gates connected in cascade form |
| <input checked="" type="radio"/> | A number of flip-flops connected in cascade |
| <input type="radio"/> | A number of latches connected in cascade form |

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)****Question # 6 of 10 (Start time: 07:25:44 PM, 08 January 2025)**

The parallel outputs of a counter circuit represent the _____

Select the correct option

<input checked="" type="radio"/>	Counter modulus
<input type="radio"/>	Parallel data word
<input type="radio"/>	Clock frequency
<input type="radio"/>	Clock count

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)****Question # 5 of 10 (Start time: 07:25:07 PM, 08 January 2025)**

Which of the following is the modified code of Excess-3 code?

Select the correct option

<input type="radio"/>	ASCII
<input type="radio"/>	BCD
<input type="radio"/>	EBDIC
<input checked="" type="radio"/>	Gray Code

CS302P - Digital Logic Design (Practical) (Semester Quiz # 04)

Question # 4 of 10 (**Start time: 07:24:25 PM, 08 January 2025**)

Comparators are used in _____

Select the correct option

<input type="radio"/>	Memory
<input type="radio"/>	Motherboard
<input checked="" type="radio"/>	CPU
<input type="radio"/>	Hard Drive

**Question # 3 of 10 (Start time: 07:23:58 PM, 08 January 2025)**

An identify comparator is defined as a digital comparator which has _____

Select the correct option

- | | |
|----------------------------------|--------------------------|
| <input type="radio"/> | No output terminals |
| <input type="radio"/> | Three output terminals |
| <input checked="" type="radio"/> | Only one output terminal |
| <input type="radio"/> | Two output terminals |

Question # 2 of 10 (**Start time: 07:23:33 PM, 08 January 2025**)

Ripple counters are also called _____

Select the correct option

<input type="radio"/>	VLSI counters
<input type="radio"/>	SSI counters
<input type="radio"/>	Synchronous counters
<input checked="" type="radio"/>	Asynchronous counters

BUTTERCUP
0324-9427076

**Question # 1 of 10 (Start time: 07:22:59 PM, 08 January 2025)**

A decimal counter has _____ states.

Select the correct option

<input type="radio"/>	2
<input type="radio"/>	9
<input type="radio"/>	7
<input checked="" type="radio"/>	10

Question # 4 of 5 (Start time: 02:40:39 AM, 03 January 2025)

Total Marks: 1

The parallel outputs of a counter circuit represent the _____

Select the correct option

 Reload Math Equations



Parallel data word



Clock frequency



Clock count



Counter modulus

Click to Save Answer & Move to Next Question

Question # 3 of 5 (Start time: 02:40:04 AM, 03 January 2025)

Total Marks: 1

Convert the binary number 1100 to Gray code.

Select the correct option

 Reload Math Equations



0111



1000



1010



0101

Click to Save Answer & Move to Next Question

Question # 2 of 5 (Start time: 02:39:23 AM, 03 January 2025)

Total Marks: 1

What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops?

Select the correct option

[Reload Math Equations](#)


<input checked="" type="radio"/>	0 to $2^n - 1$
<input type="radio"/>	0 to 2^{n+1}
<input type="radio"/>	0 to $2^n + 1$
<input type="radio"/>	0 to 2^n

[Click to Save Answer & Move to Next Question](#)

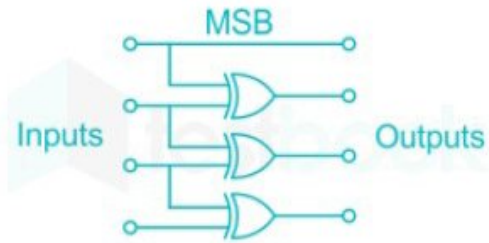Question # 1 of 5 (Start time: 02:37:31 AM, 03 January 2025)

Total Marks: 1

Following diagram is of _____ code conversion.



Select the correct option

[Reload Math Equations](#)

<input checked="" type="radio"/>	Gray
<input type="radio"/>	Excess-3
<input type="radio"/>	BCD
<input type="radio"/>	ASCII

BUTTERCUP
0324-9427076

[Click to Save Answer & Move to Next Question](#)

Question # 5 of 5 (Start time: 01:14:47 AM, 03 January 2025)

Why do we use Gray Code?

Select the correct option

- To count the number or bit changes
- Error Correction
- Invert the code
- Error Detection



Ps

AI



DELL

Question # 4 of 5 (Start time: 01:14:02 AM, 03 January 2025)


How many flop flops are required to create a counter circuit which can count from 0 to 7?

Select the correct option

- 1
- 2
- 3
- 4

BUTTERCUP

0324-9427076

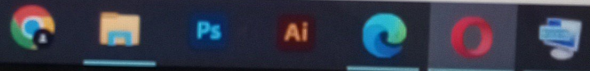

DELL

F5 F6 F7 F8 F9 F10 F11 F12

5 6 7 8 9 0

Question # 3 of 5 (Start time: 01:13:28 AM, 03 January 2025)

Which of the following is the modified code of Excess-3 code?

Select the correct option

- | | |
|----------------------------------|-----------|
| <input checked="" type="radio"/> | Gray Code |
| <input type="radio"/> | BCD |
| <input type="radio"/> | EBDIC |
| <input type="radio"/> | ASCII |



DELL

F4

F5

F6

F7

F8

F9

Question # 2 of 5 (Start time: 01:12:36 AM, 03 January 2025)

A counter circuit is usually constructed of _____

Select the correct option

- A number of NAND gates connected in cascade form
- A number of flip-flops connected in cascade
- A number of latches connected in cascade form
- A number of NOR gates connected in cascade form

DELL

Question # 1 of 5 (Start time: 01:11:53 AM, 03 January 2025)

What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops?

Select the correct option

Reload

0 to $2^n + 1$

0 to 2^n

0 to $2^n - 1$

0 to 2^{n+1}

Click to Save Answer & Move to N



DELL

Question # 10 of 10 (Start time: 11:10:55 PM, 02 January 2025)

A K-Map of size 2x2 can be used to map a _____ input boolean expression.

Select the correct option

<input checked="" type="radio"/>	2
<input type="radio"/>	4
<input type="radio"/>	3
<input type="radio"/>	1

BUTTERCUP
0324-9427076

Click to Save An

Question # 9 of 10 (Start time: 11:10:14 PM, 02 January 2025)

To

A full adder circuit takes _____ bit(s) as input and returns _____ bit(s) as output.

Select the correct option

[Reload Math E](#)

<input type="radio"/>	2, 1
<input checked="" type="radio"/>	3, 2
<input type="radio"/>	2, 2
<input type="radio"/>	3, 1

[Click to Save Answer & Move to Next Q](#)

Question # 8 of 10 (Start time: 11:09:16 PM, 02 January 2025)

Total

It should be kept in mind that don't care terms should be used along with the terms that are present in _____.

Select the correct option

[Reload Math Equ](#)

<input type="radio"/>	Expressions
<input checked="" type="radio"/>	K-Map
<input type="radio"/>	Minterms
<input type="radio"/>	Latches

[Click to Save Answer & Move to Next Que](#)

Question # 7 of 10 (Start time: 11:08:46 PM, 02 January 2025)

Each product term of a group, $w'xy'$ and wy , represents the _____ in that group.

Select the correct option



<input type="radio"/>	Sum of Maxterms
<input type="radio"/>	POS
<input checked="" type="radio"/>	Sum of Minterms
<input type="radio"/>	Input

Click to Save Answer &

Question # 6 of 10 (Start time: 11:08:11 PM, 02 January 2025)

Don't care conditions can be used for simplifying Boolean expressions in _____.

Select the correct option

- | | |
|----------------------------------|-----------|
| <input type="radio"/> | Terms |
| <input checked="" type="radio"/> | K-maps |
| <input type="radio"/> | Registers |
| <input type="radio"/> | Latches |

[Click to Save A](#)

Question # 5 of 10 (Start time: 11:06:47 PM, 02 January 2025)

Which of the following is not a valid number for grouping of terms in K-Map?

Select the correct option

- | | |
|----------------------------------|---|
| <input type="radio"/> | 1 |
| <input type="radio"/> | 4 |
| <input checked="" type="radio"/> | 2 |
| <input type="radio"/> | 3 |

Question # 4 of 10 (Start time: 11:05:58 PM, 02 January 2025)

Total Marks: 1

A half adder can be built by using the combination of _____ and _____ gates.

Select the correct option

[Reload Math Equations](#)

<input checked="" type="radio"/>	AND, XOR
<input type="radio"/>	OR, XOR
<input type="radio"/>	AND, NOT
<input type="radio"/>	AND, OR

BUTTERCUP
0324-9427076

[Click to Save Answer & Move to Next Question](#)

Question # 2 of 10 (Start time: 11:04:54 PM, 02 January 2025)

Total Marks: 1

When implementing a half adder by using gates, which of the following gates is used to give Sum (S) as an output?

Select the correct option

[Reload Math Equations](#)

NOR



AND



XOR



OR

[Click to Save Answer & Move to Next Question](#)

Question # 1 of 10 (Start time: 11:04:30 PM, 02 January 2025)

Total number of inputs in a half adder is _____.

Select the correct option

<input type="radio"/>	1
<input checked="" type="radio"/>	2
<input type="radio"/>	4
<input type="radio"/>	3

BUTTERCUP
0324-9427076

Question # 10 of 10 (Start time: 10:55:42 PM, 02 January 2025)

The K-map based Boolean reduction is based on the following Unifying Theorem: $A + A' = 1$.

Select the correct option



<input type="radio"/>	Impact
<input checked="" type="radio"/>	Complementarity
<input type="radio"/>	Force
<input type="radio"/>	Non Impact

Click to Save Answer & Move

Question # 9 of 10 (Start time: 10:54:49 PM, 02 January 2025)

Total Marks: 10

It should be kept in mind that don't care terms should be used along with the terms that are present in _____.

Select the correct option

[Reload Math Equation](#)

<input checked="" type="radio"/>	Expressions
<input type="radio"/>	Minterms
<input type="radio"/>	Latches
<input type="radio"/>	K-Map

[Click to Save Answer & Move to Next Question](#)

Question # 8 of 10 (Start time: 10:53:47 PM, 02 January 2025)

Total Marks:

In 8x1 multiplexer, which one of the following lines must always be connected to ground in order to activate the mutiplexer?

Select the correct option

[Reload Math Equations](#)

<input checked="" type="radio"/>	G'
<input type="radio"/>	V _{cc}
<input type="radio"/>	Y
<input type="radio"/>	W

[Click to Save Answer & Move to Next Question](#)

Question # 7 of 10 (**Start time: 10:52:59 PM, 02 January 2025**)

Which of the following symbols is used to represent XOR operation?

Select the correct option

<input type="radio"/>	+
<input type="radio"/>	\wedge
<input checked="" type="radio"/>	\oplus
<input type="radio"/>	X

Click to

Question # 6 of 10 (**Start time: 10:52:23 PM, 02 January 2025**)

There are _____ cells in a 4-variable K-map.

Select the correct option

<input type="radio"/>	8
<input type="radio"/>	20
<input checked="" type="radio"/>	16
<input type="radio"/>	24

Question # 5 of 10 (Start time: 10:51:51 PM, 02 January 2025)

Total Marks: 1

When implementing a half adder by using gates, which of the following gates is used to return carry bit as an output?

Select the correct option

[Reload Math Equations](#)

AND



XOR



OR



NAND

BUTTERCUP

0324-9427076

[Click to Save Answer & Move to Next Question](#)

Question # 4 of 10 (Start time: 10:51:02 PM, 02 January 2025)

Which of the following is not a valid number for grouping of terms in K-Map?

Select the correct option

- | | |
|----------------------------------|---|
| <input checked="" type="radio"/> | 3 |
| <input type="radio"/> | 4 |
| <input type="radio"/> | 2 |
| <input type="radio"/> | 1 |

Question # 3 of 10 (Start time: 10:49:58 PM, 02 January 2025)

Total Marks

When implementing a half adder by using gates, which of the following gates is used to give Sum (S) as an output?

Select the correct option

 Reload Math Equation

AND

XOR

NOR

OR

Click to Save Answer & Move to Next Question

Question # 2 of 10 (Start time: 10:48:52 PM, 02 January 2025)

Consider a 3-variable Karnaugh Map. How many groups of 1's can be made from the below given Karnaugh Map?

A/BC	00	01	11	10
0	0	1	1	0
1	1	1	1	1

Select the correct option

 Reload Math

<input checked="" type="radio"/>	1
<input type="radio"/>	4
<input type="radio"/>	2
<input type="radio"/>	6

BUTTERCUP
0324-9427076

Click to Save Answer & Move to Next

Question # 1 of 10 (Start time: 10:48:10 PM, 02 January 2025)

In order to build an XOR gate using NAND gates only, ----- gate(s) are required.

Select the correct option



<input type="radio"/>	2
<input type="radio"/>	3
<input checked="" type="radio"/>	4
<input type="radio"/>	1


Click to Save Answer &

Question # 10 of 10 (Start time: 12:25:03 PM, 02 January 2025)

Total Marks: 1

When implementing a half adder by using gates, which of the following gates is used to return carry bit as an output?

Select the correct option

 Reload Math Equations

XOR

AND

NAND

OR

CS302P - Digital Logic Design (Practical) (Semester Quiz # 03)

Question # 7 of 10 (Start time: 12:21:47 PM, 02 January 2025)

It should be kept in mind that don't care terms should be used along with the terms that are present in

Select the correct option

- | | |
|----------------------------------|-------------|
| <input type="radio"/> | Latches |
| <input type="radio"/> | Expressions |
| <input checked="" type="radio"/> | Minterms |
| <input type="radio"/> | K-Map |

BUTTERCUP
0324-9427076

CS302P - Digital Logic Design (Practical) (Semester Quiz # 03)


Question # 8 of 10 (Start time: 12:22:43 PM, 02 January 2025)

There are _____ cells in a 5-variable K-map.

Select the correct option:

- | | |
|----------------------------------|----|
| <input type="radio"/> | 64 |
| <input type="radio"/> | 16 |
| <input type="radio"/> | 24 |
| <input checked="" type="radio"/> | 32 |

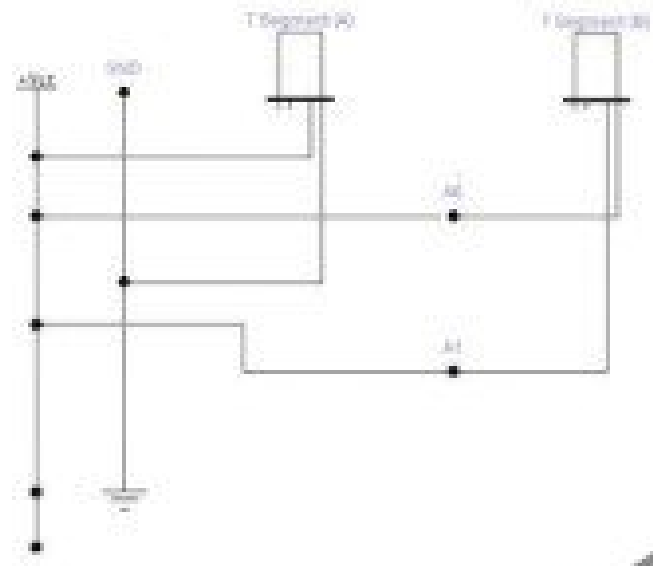Consider the below given EWB circuit, what values will be displayed on 7-segment displays A and B when the circuit simulation is activated in EWB?



BUTTERCUP
0324-9427076

Select the correct option

- 1, 3
- 3, 3
- 2, 3
- 0, 1

Question # 6 of 10 (Start time: 12:21:02 PM, 02 January 2025)

A K-Map of size 2x2 can be used to map a input boolean expression.

Select the correct option

- | | |
|----------------------------------|---|
| <input checked="" type="radio"/> | 4 |
| <input type="radio"/> | 3 |
| <input type="radio"/> | 2 |
| <input type="radio"/> | 1 |

Question # 3 of 10 (Start time: 12:16:59 PM, 02 January 2025)

Each product term of a group, $w'xy'$ and wy , represents the in that group.

Select the correct option

- | | |
|----------------------------------|-----------------|
| <input type="radio"/> | Sum of Maxterms |
| <input checked="" type="radio"/> | Sum of Minterms |
| <input type="radio"/> | input |
| <input type="radio"/> | POS |

Consider a 3-variable Karnaugh Map. How many groups of 1s can be made from the below given Karnaugh Map?

A/BC	00	01	11	10
0	0	1	1	0
1	1	1	1	1

Select the correct option

1

4

6

2

Question # 2 of 10 (**Start time: 12:16:29 PM, 02 January 2025**)

How many select lines would be required for an 8x1 multiplexer?

Select the correct option

- | | | |
|----------------------------------|---|--------------|
| <input type="radio"/> | 8 | BUTTERCUP |
| <input type="radio"/> | 1 | 0324-9427076 |
| <input checked="" type="radio"/> | 3 | |
| <input type="radio"/> | 2 | |

Question # 1 of 10 (Start time: 12:16:02 PM, 03 January 2025)

Each group of adjacent Minterms (group size in powers of twos) corresponds to a possible product term of the given

Select the correct option

- | | |
|----------------------------------|----------|
| <input type="radio"/> | Word |
| <input checked="" type="radio"/> | Function |
| <input type="radio"/> | Value |
| <input type="radio"/> | Set |

Question # 1 of 5 (Start time: 02:48:28 AM, 27 December 2024)

Total Marks: 1

The parallel outputs of a counter circuit represent the -----

Select the correct option

 Reload Math Equations

<input checked="" type="radio"/>	Clock count
<input type="radio"/>	Parallel data word
<input type="radio"/>	Clock frequency
<input type="radio"/>	Counter modulus


Click to Save Answer & Move to Next Question

Question # 2 of 5 (Start time: 02:48:59 AM, 27 December 2024)

Total Marks:

Three decade counter would have -----

Select the correct option

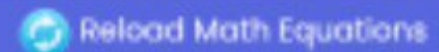 Reload Math Equations



5 BCD counters



4 BCD counters



2 BCD counters



3 BCD counters

BUTTERCUP
0324-9427076

Click to Save Answer & Move to Next Question

Question # 3 of 5 (Start time: 02:49:21 AM, 27 December 2024)

Total Marks: 1

A counter circuit is usually constructed of -----

Select the correct option

 Reload Math Equations

A number of NAND gates connected in cascade form

A number of latches connected in cascade form

A number of flip-flops connected in cascade

A number of NOR gates connected in cascade form

BUTTERCUP

0324-9427076

Click to Save Answer & Move to Next Question

Question # 4 of 5 (Start time: 02:49:52 AM, 27 December 2024)

Total Marks: 1

How many select lines would be required for an 8x1 multiplexer?

Select the correct option

 Reload Math Equations



6



1



3



2

BUTTERCUP
0324-9427076

Click to Save Answer & Move to Next Question

Question # 1 of 5 (Start time: 02:52:38 AM, 27 December 2024)

Total Marks:

In 8x1 multiplexer, which one of the following lines must always be connected to ground in order to activate the multiplexer?

Select the correct option

[Reload Math Equations](#)

W

Y

G'

Vcc

BUTTERCUP
0324-9427076

[Click to Save Answer & Move to Next Question](#)

Question # 2 of 5 (Start time: 02:53:18 AM, 27 December 2024)

Total Marks:

The parallel outputs of a counter circuit represent the -----

Select the correct option

[Reload Math Equations](#)

Clock count



Clock frequency



Parallel data word



Counter modulus

[Click to Save Answer & Move to Next Question](#)

Question # 3 of 5 (Start time: 02:53:40 AM, 27 December 2024)

Total Marks: 1

Ripple counters are also called -----

Select the correct option

 Reload Math Equations

- Asynchronous counters
- SSI counters
- VLSI counters
- Synchronous counters

BUTTERCUP
0324-9427076

Click to Save Answer & Move to Next Question

Question # 4 of 5 (Start time: 02:54:04 AM, 27 December 2024)

Total Marks: 1

How many select lines would be required for an 8x1 multiplexer?

Select the correct option

 Reload Math Equations



1



3



8



2

BUTTERCUP
0324-9427076

Click to Save Answer & Move to Next Question

Question # 5 of 5 (Start time: 02:54:28 AM, 27 December 2024)

Total Marks:

A counter circuit is usually constructed of -----

Select the correct option

[Reload Math Equations](#)

- | | |
|----------------------------------|--|
| <input type="radio"/> | A number of NAND gates connected in cascade form |
| <input type="radio"/> | A number of latches connected in cascade form |
| <input checked="" type="radio"/> | A number of flip-flops connected in cascade |
| <input type="radio"/> | A number of NOR gates connected in cascade form |

[Click to Save Answer & Move to Next Question](#)



CS302P
LAB QUIZZES
FINAL TERM
FALL 2024
BY
BUTTERCUP
FOR LMS HANDLING
CONTACT
0324-9427076
THE BRAINY SQUAD