

Cs 302 Mid Term

Objective Type

Prepared By.....**Talha Goraya**

If you found any mistake plz feedback at
whatsapp 03401213047 & Email at
talhagoraya2000@gmail.com

Please choose one

A SOP expression is equal to 1 _____

- ▶ All the variables in domain of expression are present
- ▶ At least one variable in domain of expression is present.
- ▶ When one or more product terms in the expression are equal to 0.
- ▶ **When one or more product terms in the expression are equal to 1**

- Please choose one

The output $A < B$ is set to 1 when the input combinations is _____

- ▶ A=10, B=01
- ▶ A=11, B=01
- ▶ A=01, B=01
- ▶ **A=01, B=10**

) - **Please choose one**

Two 2-bit comparator circuits can be connected to form single 4-bit comparator

▶ **True**

▶ False

- **Please choose one**

High level Noise Margins (VNH) of CMOS 5 volt series circuits is

▶ 0.3 V

▶ 0.5 V

▶ **0.9 V (**

▶ 3.3 V

Please choose one

If we multiply “723” and “34” by representing them in floating point notation i.e. by first, converting them in floating point representation and then multiplying them, the value of mantissa of result will be _____

▶ **24.582 (But not sure)**

▶ 2.4582

▶ 24582

▶ 0.24582

Please choose one

The output of the expression $F=A+B+C$ will be Logic _____ when $A=0, B=1, C=1$. the symbol “+” here represents OR Gate.

▶ Undefined

▶ **One**

▶ Zero

- ▶ 10 (binary)

Please choose one

If an active-HIGH S-R latch has a 0 on the S input and a 1 on the R input and then the R input goes to 0, the latch will be

_____.

- ▶ **SET (**
- ▶ RESET
- ▶ Clear
- ▶ Invalid

Please choose one

3.3 v CMOS series is characterized by _____ and _____ as compared to the 5 v CMOS series.

- ▶ Low switching speeds, high power dissipation
- ▶ Fast switching speeds, high power dissipation
- ▶ **Fast switching speeds, very low power dissipation**
- ▶ Low switching speeds, very low power dissipation

Please choose one

The binary value “1010110” is equivalent to decimal _____

- ▶ **86 (According to Formula)**
- ▶ 87
- ▶ 88
- ▶ 89

Please choose one

The _____ Encoder is used as a keypad encoder.

- ▶ 2-to-8 encoder
- ▶ 4-to-16 encoder

- ▶ BCD-to-Decimal
- ▶ **Decimal-to-BCD Priority**

Please choose one

"Sum-of-Weights" method is used _____

- ▶ **to convert from one number system to other (**
- ▶ to encode data
- ▶ to decode data
- ▶ to convert from serial to parallel data

- Please choose one

The maximum number that can be represented using unsigned octal system is _____

- ▶ 1
- ▶ **7**
- ▶ 9
- ▶ 16

- Please choose one

If we add "723" and "134" by representing them in floating point notation i.e. by first, converting them in floating point representation and then adding them, the value of exponent of result will be _____

- ▶ 0
- ▶ 1
- ▶ **2**
- ▶ 3

Please choose one

The diagram given below represents _____

- ▶ Demorgans law
- ▶ Associative law
- ▶ **Product of sum form (According to rule of theorem)**
- ▶ Sum of product form

Please choose one

For a 3-to-8 decoder how many 2-to-4 decoders will be required?

- ▶ **2**
- ▶ 1
- ▶ 3
- ▶ 4

- Please choose one

GAL is an acronym for _____.

- ▶ Giant Array Logic
- ▶ **General Array Logic**
- ▶ Generic Array Logic
- ▶ Generic Analysis Logic

- Please choose one

The Quad Multiplexer has _____ outputs

- ▶ **4**
- ▶ 8
- ▶ 12
- ▶ 16

Please choose one

$A.(B.C) = (A.B).C$ is an expression of _____

- ▶ Demorgan's Law
- ▶ Distributive Law
- ▶ Commutative Law

▶ **Associative Law (**

Please choose one

2's complement of any binary number can be calculated by

- ▶ adding 1's complement twice
- ▶ **adding 1 to 1's complement (**
- ▶ subtracting 1 from 1's complement.
- ▶ calculating 1's complement and inverting Most significant bit

Please choose one

The binary value “1010110” is equivalent to decimal _____

▶ **86 (According to formula)**

- ▶ 87
- ▶ 88
- ▶ 89

Please choose one

Tri-State Buffer is basically a/an _____ gate.

- ▶ AND
- ▶ OR
- ▶ NOT
- ▶ **XOR (**

The binary value “11011” is equivalent to _____

▶ **1B (According to rule)**

- ▶ 1C
- ▶ 1D
- ▶ 1E

. An important application of AND Gate is its use in counter circuit

- ▶ **True (**
- ▶ False

The OR Gate performs a Boolean _____ function

- ▶ **Addition**
- ▶ Subtraction
- ▶ Multiplication
- ▶ Division

TTL based devices work with a dc supply of ____ Volts

- ▶ +10
- ▶ **+5**
- ▶ +3
- ▶ 3.3

A standard POS form has _____ terms that have all the variables in the domain of the expression.

- ▶ **Sum**
- ▶ Product
- ▶ Min
- ▶ Composite

. A SOP expression having a domain of 3 variables will have a truth table having _____ combinations of inputs and corresponding output values.

- ▶ 2
- ▶ 4
- ▶ **8 (According to rule)**

▶ 16

A BCD to 7-Segment decoder has

- ▶ 3 inputs and 7 outputs
- ▶ **4 inputs and 7 outputs)**
- ▶ 7 inputs and 3 outputs
- ▶ inputs and 4 outputs

. In the Karnaugh map shown above, which of the loops shown represents a legal grouping?

- ▶ A
- ▶ ▶
- ▶ **C**
- ▶ D

The binary value of 1010 is converted to the product term

- ▶ True
- ▶ **False**

10. The binary numbers A = 1100 and B = 1001 are applied to the inputs of a comparator. What are the output levels?

- ▶ $A > B = 1, A < B = 0, A = B = 1$
- ▶ $A > B = 0, A < B = 1, A = B = 0$
- ▶ **$A > B = 1, A < B = 0, A = B = 0$**
- ▶ $A > B = 0, A < B = 1, A = B = 1$

If an active-HIGH S-R latch has a 0 on the S input and a 1 on the R input and then the R input goes to 0, the latch will be _____.

- ▶ **SET ()**
- ▶ RESET
- ▶ Clear
- ▶ Invalid

. Consider a circuit consisting of two consecutive NOT gates, the entire circuit belongs to a CMOS 5 Volt series, if certain voltage is applied on the input, the output voltage of Logic high signal (VoH) will be in the range of _____ volts.

- ▶ 4 to 4.5
- ▶ **4.5 to 5**
- ▶ 0 to 4.5
- ▶ 0 to 3.5

. $A.(B.C) = (A.B).C$ is an expression of _____

- ▶ Demorgan's Law
- ▶ Distributive Law
- ▶ Commutative Law
- ▶ **Associative Law**

The 4-bit 2's complement representation of "+5" is _____

- ▶ 1010
- ▶ 1110
- ▶ **1011**
- ▶ 0101

Which of the number is not a representative of hexadecimal system

- ▶ 1234
- ▶ ABCD

▶ 1001

Please choose one

- ▶ 1
- ▶ 7
- ▶ 9
- ▶ 16

- Please choose one

The 3-variable Karnaugh Map (K-Map) has _____ cells for min or max terms

- ▶ 4
- ▶ **8**
- ▶ 12
- ▶ 16

Please choose one

The binary numbers $A = 1100$ and $B = 1001$ are applied to the inputs of a comparator. What are the output levels?

- ▶ $A > B = 1, A < B = 0, A = B = 1$
- ▶ $A > B = 0, A < B = 1, A = B = 0$
- ▶ **$A > B = 1, A < B = 0, A = B = 0$**
- ▶ $A > B = 0, A < B = 1, A = B = 1$

) - Please choose one

A particular Full Adder has

- ▶ **3 inputs and 2 output**
- ▶ 3 inputs and 3 output
- ▶ 2 inputs and 3 output

▶ 2 inputs and 2 output

- Please choose one

The function to be performed by the processor is selected by set of inputs known as _____

▶ **Function Select Inputs**

▶ MicroOperation selectors

▶ OP CODE Selectors

▶ None of given option

Please choose one

For a 3-to-8 decoder how many 2-to-4 decoders will be required?

▶ **2 (**

▶ 1

▶ 3

▶ 4

- Please choose one

GAL is an acronym for _____.

▶ Giant Array Logic

▶ **General Array Logic (**

▶ Generic Array Logic

▶ Generic Analysis Logic

Please choose one

The Quad Multiplexer has _____ outputs

▶ **4**

▶ 8

▶ 12

▶ **16**

) - **Please choose one**

A.(B.C) = (A.B).C is an expression of _____

- ▶ Demorgan's Law
- ▶ Distributive Law
- ▶ Commutative Law
- ▶ **Associative Law (**

- **Please choose one**

2's complement of any binary number can be calculated by

- ▶ adding 1's complement twice
- ▶ **adding 1 to 1's complement**
- ▶ subtracting 1 from 1's complement.
- ▶ calculating 1's complement and inverting Most significant bit

- **Please choose one**

The binary value "1010110" is equivalent to decimal _____

- ▶ **86 (According to formula)**
- ▶ 87
- ▶ 88
- ▶ 89

- **Please choose one**

Tri-State Buffer is basically a/an _____ gate.

- ▶ AND
- ▶ OR
- ▶ **NOT**
- ▶ XOR

- **Please choose one**

GAL can be reprogrammed because instead of fuses _____ logic is

used in it

- ▶ **E2CMOS**
- ▶ TTL
- ▶ CMOS+
- ▶ **None of the given options**

Please choose one

The device shown here is most likely a

- ▶ Comparator
- ▶ **Multiplexer click here for detail**
- ▶ Demultiplexer
- ▶ Parity generator

Please choose one

If "1110" is applied at the input of BCD-to-Decimal decoder which output pin will be activated:

- ▶ 2nd
- ▶ 4th
- ▶ 14th
- ▶ **No output wire will be activated**

- Please choose one

Half-Adder Logic circuit contains 2 XOR Gates

- ▶ True
- ▶ **False**

- Please choose one

A particular Full Adder has

- ▶ **3 inputs and 2 output**
- ▶ 3 inputs and 3 output

- ▶ 2 inputs and 3 output
- ▶ **2 inputs and 2 output**

- Please choose one

Sum = $A \oplus B \oplus C$ CarryOut = $C(A \oplus B) + AB$
are the Sum and CarryOut expression of

- ▶ Half Adder
- ▶ **Full Adder**
- ▶ 3-bit parallel adder
- ▶ MSI adder circuit

Please choose one

A Karnaugh map is similar to a truth table because it presents all the possible values of input variables and the resulting output of each value.

- ▶ **True click here for detail**
- ▶ False

Please choose one

The output $A < B$ is set to 1 when the input combinations is

- ▶ A=10, B=01
- ▶ A=11, B=01
- ▶ A=01, B=01
- ▶ **A=01, B=10**

Please choose one

The 4-variable Karnaugh Map (K-Map) has _____ cells for min or max terms

- ▶ 4
- ▶ 8
- ▶ 12

▶ **16**

- Please choose one

Generally, the Power dissipation of devices remains constant throughout their operation.

▶ **TTL**

▶ CMOS 3.5 series

▶ CMOS 5 Series

▶ **Power dissipation of all circuits increases with time.**

- Please choose one

The decimal "8" is represented as using Gray-Code.

▶ 0011

▶ **1100**

▶ 1000

▶ 1010

Please choose one

$(A+B).(A+C) =$

▶ B+C

▶ **A+BC**

▶ AB+C

▶ AC+B

- Please choose one

$A.(B+ C) = A.B + A.C$ is the expression of

▶ Demorgan's Law

▶ Commutative Law

▶ **Distributive Law**

▶ Associative Law

Please choose one

NOR Gate can be used to perform the operation of AND, OR and NOT Gate

▶ **FALSE**

▶ **TRUE**

In ANSI/IEEE Standard 754 “Mantissa” is represented by 32-bits bits

▶ 8-bits

▶ 16-bits

▶ **32-bits**

▶ 64-bits

- Please choose one

Caveman number system is Base _5 number system

▶ 2

▶ **5**

▶ 10

▶ 16

- Please choose one

According to Demorgan’s theorem:

▶ A.B.C

▶

▶ **(Page 74)**

▶

- Please choose one

The Extended ASCII Code (American Standard Code for Information Interchange) is a _____ code

- \▶ 2-bit
- ▶ 7-bit
- ▶ **8-bit**
- ▶ 16-bit

) - **Please choose one**

The AND Gate performs a logical _____ function

- ▶ Addition
- ▶ Subtraction
- ▶ **Multiplication**
- ▶ Division

Please choose one

NOR gate is formed by connecting _____

- ▶ **OR Gate and then NOT Gate**
- ▶ NOT Gate and then OR Gate
- ▶ AND Gate and then OR Gate
- ▶ OR Gate and then AND Gate

Please choose one

Generally, the Power dissipation of _____ devices remains constant throughout their operation.

- ▶ **TTL**
- ▶ CMOS 3.5 series
- ▶ CMOS 5 Series
- ▶ Power dissipation of all circuits increases with time.

Please choose one

Two 2-bit comparator circuits can be connected to form single 4-bit comparator

▶ **True**

▶ False

Please choose one

When the control line in tri-state buffer is high the buffer operates like a _____ gate

▶ AND

▶ OR

▶ **NOT (**

▶ XOR

- Please choose one

The GAL22V10 has _____ inputs

▶ **22**

▶ 10

▶ 44

▶ 20

- Please choose one

The ABEL symbol for “OR” operation is

▶ !

▶ &

▶ **#**

▶ \$

- Please choose one

The OLMC of the GAL16V8 is _____ to the OLMC of the GAL22V10

▶ Similar

▶ Different

▶ **Similar with some enhancements**

- ▶ Depends on the type of PALs input size

Please choose one

All the ABEL equations must end with _____

- ▶ “ . “ (a dot)
- ▶ “ \$ “ (a dollar symbol)
- ▶ “ ; “ (a semicolon)
- ▶ “ endl “ (keyword “endl”)

Please choose one

The Quad Multiplexer has _____ outputs

- ▶ 4 (
- ▶ 8
- ▶ 12
- ▶ 16

- Please choose one

"Sum-of-Weights" method is used _____

- ▶ to convert from one number system to other)
- ▶ to encode data
- ▶ to decode data
- ▶ to convert from serial to parralel data

Please choose one

A latch has _____ stable states

- ▶ One
- ▶ Two)
- ▶ Three
- ▶ Four

- Please choose one

Sequential circuits have storage elements

▶ **True**

▶ False

Please choose one

The ABEL symbol for “XOR” operation is

▶ **\$**

▶ #

▶ !

▶ &

- Please choose one

A Demultiplexer is not available commercially.

▶ **True**

▶ False

Please choose one

Using multiplexer as parallel to serial converter requires _____
connected to the multiplexer

▶ **A parallel to serial converter circuit**

▶ A counter circuit

▶ A BCD to Decimal decoder

▶ A 2-to-8 bit decoder

- Please choose one

The device shown here is most likely a

▶ Comparator

▶ **Multiplexer click here for detail**

▶ Demultiplexer

- ▶ Parity generator

Please choose one

The main use of the Multiplexer is to

▶ Select data from multiple sources and to route it to a single Destination (Page 167)

- ▶ Select data from Single source and to route it to a multiple Destinations
- ▶ Select data from Single source and to route to single destination
- ▶ Select data from multiple sources and to route to multiple destinations

- Please choose one

A logic circuit with an output consists of _____.

- ▶ two AND gates, two OR gates, two inverters
- ▶ three AND gates, two OR gates, one inverter
- ▶ two AND gates, one OR gate, two inverters**
- ▶ two AND gates, one OR gate

Please choose one

The binary value of 1010 is converted to the product term

- ▶ True
- ▶ False**

Please choose one

The 3-variable Karnaugh Map (K-Map) has _____ cells for min or max terms

- ▶ 4
- ▶ 8**
- ▶ 12
- ▶ 16

Please choose one

Following is standard POS expression

▶ **True (According to logic)**

▶ False

Please choose one

The output of the expression $F=A+B+C$ will be Logic _____ when $A=0, B=1, C=1$. the symbol "+" here represents OR Gate.

▶ Undefined

▶ **One**

▶ Zero

▶ 10 (binary)

Please choose one

The Extended ASCII Code (American Standard Code for Information Interchange) is a _____ code

▶ 2-bit

▶ 7-bit

▶ **8-bit**

▶ 16-bit

- Please choose one

The diagram given below represents _____

▶ Demorgans law

▶ Associative law

▶ **Product of sum form (According to rule)**

▶ Sum of product form

Please choose one

The diagram given below represents _____

- ▶ Demorgans law
- ▶ Associative law
- ▶ Product of sum form
- ▶ **Sum of product form**

Please choose one

The output of an AND gate is one when _____

- ▶ **All of the inputs are one**
- ▶ Any of the input is one
- ▶ Any of the input is zero
- ▶ All the inputs are zero

Please choose one

The 4-variable Karnaugh Map (K-Map) has _____ cells for min or max terms

- ▶ 4
- ▶ 8
- ▶ 12
- ▶ **16)**

Please choose one

A BCD to 7-Segment decoder has

- ▶ 3 inputs and 7 outputs
- ▶ **4 inputs and 7 outputs**
- ▶ 7 inputs and 3 outputs
- ▶ 7 inputs and 4 outputs

Please choose one

Two 2-input, 4-bit multiplexers 74X157 can be connected to implement

a ____ multiplexer.

- ▶ 4-input, 8-bit
- ▶ 4-input, 16-bit
- ▶ 2-input, 8-bit
- ▶ **2-input, 4-bit**

- Please choose one

The PROM

consists of a fixed non-programmable _____ Gate array configured as a decoder.

- ▶ **AND**
- ▶ OR
- ▶ NOT
- ▶ XOR

Please choose one

In ABEL the variable „A“ is treated separately from variable „a“

- ▶ **True**
- ▶ False

Please choose one

The ABEL notation equivalent to Boolean expression $A+B$ is:

- ▶ A & B
- ▶ A ! B
- ▶ **A # B**
- ▶ A \$ B

L-21

Please choose one

If an active-HIGH S-R latch has a 0 on the S input and a 1 on the R input and then the R input goes to 0, the latch will be

-
- ▶ **SET**
 - ▶ RESET
 - ▶ Clear
 - ▶ Invalid

Please choose one

Demultiplexer has

- ▶ Single input and single outputs.
- ▶ Multiple inputs and multiple outputs.
- ▶ **Single input and multiple outputs.**
- ▶ Multiple inputs and single output.

- Please choose one

Which one is true:

- ▶ **Power consumption of TTL is higher than of CMOS**
- ▶ Power consumption of CMOS is higher than of TTL
- ▶ Both TTL and CMOS have same power consumption
- ▶ Power consumption of both CMOS and TTL depends on no. of gates in the circuit.

Please choose one

The first Least Significant digit in decimal number system has

position 0 and weight equal to 1

position 1 and weight equal to 0

position 1 and weight equal to 10

position 0 and weight equal to 10

Please choose one

The decimal equivalent of the binary number “10011” is

19 (According to rule)

99

29

None of given options

Please choose one

In ANSI/IEEE Standard 754 “Mantissa” is represented by 32-bits bits

▶ 8-bits

▶ 16-bits

▶ **32-bits**

▶ 64-bits

Please choose one

The binary value “11011” is equivalent to

1B (According to rule)

1C

1D

1E

- Please choose one

NOR gate is formed by connecting

OR Gate and then NOT Gate

NOT Gate and then OR Gate

AND Gate and then OR Gate

OR Gate and then AND Gate

- Please choose one

“74ALS” stands for

Advanced Low-frequency Schottky TTL

Advanced Low-dissipation Schottky TTL

Advanced Low-Power Schottky TTL

Advanced Low-propagation Schottky TTL

- Please choose one

An adder circuit can be used to perform subtraction operation

True

False

Please choose one

For a 3-to-8 decoder how many 2-to-4 decoders will be required?

2)

3 4 1

Please choose one

3-to-8 decoder can be used to implement Standard SOP and POS Boolean expressions

True

False

- Please choose one

Two 2-input, 4-bit multiplexers 74X157 can be connected to implement a multiplexer.

2-input, 4-bit

4-input, 8-bit

4-input, 16-bit

2-input, 8-bit

Please choose one

The four outputs of two 4-input multiplexers, connected to form a 16-input multiplexer, are connected together through a 4-input gate

AND

OR

NAND

XOR

- Please choose one

The Programmable Array Logic (PAL) has AND array and a OR array

Fixed, programmable

Programmable, fixed

Fixed, fixed

Programmable, programmable

Please choose one

Sequential circuits have storage elements

True

False

Please choose one

Demultiplexer has

Single input and single outputs.

Multiple inputs and multiple outputs.

Single input and multiple outputs.

Multiple inputs and single output.

Prepared By..... Talha Goraya

If you found any mistake plz feedback at

whatsapp 03401213047 & Email at

talhagoraya2000@gmail.com

