

Question No : 1 of 26

Marks: 1 (Budgeted Time 1 Min)

The range of Excess-8 code is from _____ to _____.

Answer (Please select your correct option)

+7 to -8

correct

+8 to -7

+9 to -8

-9 to +8

Made By: Waqar Siddhu

Question No : 2 of 26

Marks: 1 (Budgeted Time 1 Min)

The decimal "17" in BCD will be represented as _____.

Answer (Please select your correct option)

11101

11011

10111

correct

11110

Made By: Waqar Siddhu

Question No : 3 of 26

Marks: 1 (Budgeted Time 1 Min)

The four outputs of two 4-input multiplexers, connected to form a 16-input multiplexer, are connected together through a 4-input _____ gate

Answer (Please select your correct option)

AND

OR

correct

NAND

XOR

Made By: Waqar Siddhu

Question No : 4 of 26

Marks: 1 (Budgeted Time 1 Min)

A standard interface for programming the In-System PLD consists of _____.

Answer (Please select your correct option)

2-wire

4-wire

correct

8-wire

16-wire

Made By: Waqar Siddhu

Question No : 5 of 26

Marks: 1 (Budgeted Time 1 Min)

_____ Dual, 4-input multiplexer can be connected to form a 16-input multiplexer.

Answer (Please select your correct option)

2

3

4

correct

5

Made By: Waqar Siddhu

Question No : 6 of 26

Marks: 1 (Budgeted Time 1 Min)

S-R latch can be implemented by using _____ gates

Answer (Please select your correct option)

AND, OR

correct

NAND, NOR

NAND, XOR

NOT, XOR

Made By: Waqar Siddhu

Question No : 7 of 26

Marks: 1 (Budgeted Time 1 Min)

A product term is 0 when _____.

Answer (Please select your correct option)

Any of the literals is 1

At least two literals are 1

All the literals are 1

Any of the literal is 0

correct

Made By: Waqar Siddhu

Question No : 8 of 26

Marks: 1 (Budgeted Time 1 Min)

What will be the output of a 3-input NAND gate for the input values: A=1, B=0, C=1

Answer (Please select your correct option)

Zero

One

Undefined

No output, as input is invalid

correct

Made By: Waqar Siddhu

Question No : 9 of 26

Marks: 1 (Budgeted Time 1 Min)

_____ is not a valid hexadecimal number.

Answer (Please select your correct option)

1234

ABCD

1001

DEHF

correct

Made By: Waqar Siddhu

Question No : 10 of 26

Marks: 1 (Budgeted Time 1 Min)

2's complement of any binary number can be calculated by

Answer (Please select your correct option)

- adding 1 to 1's complement **correct**
- subtracting 1 from 1's complement.
- calculating 1's complement and inverting Most significant bit
- adding 1's complement twice

Made By: Waqar Siddhu

Question No : 11 of 26

Marks: 1 (Budgeted Time 1 Min)

A BCD to 7-Segment decoder has _____ inputs and _____ outputs.

Answer (Please select your correct option)

- 3, 7
- 4, 7 **correct**
- 7, 3
- 7, 4

Made By: Waqar Siddhu

Question No : 12 of 26

Marks: 1 (Budgeted Time 1 Min)

Which of the following simplification method is intended to be used for Boolean expressions having more than four variables?

Answer (Please select your correct option)

- Boolean Algebra and rules
- Karnaugh Map
- Quine-McCluskey **correct**
- Demorgan's Theorem

Made By: Waqar Siddhu

Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)

In the following Karnaugh map, which group has "legal grouping" ?



Answer (Please select your correct option)

A

C

B

C

C

correct


D

C

Made By: Waqar Siddhu

Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)

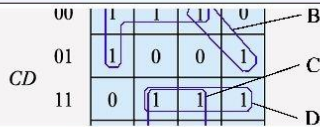

Answer (Please select your correct option)

A

C

B

C

C

C


D

C

Made By: Waqar Siddhu

Question No : 13 of 26

Marks: 1 (Budgeted Time 1 Min)

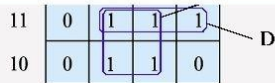

Answer (Please select your correct option)

A

C

B

C

C

C

D

C

Made By: Waqar Siddhu

Question No : 14 of 26

Marks: 1 (Budgeted Time 1 Min)

What are the values of sum and carry out when two 4-bit binary numbers (1011 and 1111) are applied to a 4-bit parallel adder and carry input is 1.

Answer (Please select your correct option)

$\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 0111, C_{out} = 0$

$\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 1111, C_{out} = 1$

$\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 1011, C_{out} = 1$

$\Sigma_4 \Sigma_3 \Sigma_2 \Sigma_1 = 1100, C_{out} = 1$

Made By: Waqar Siddhu

Question No : 15 of 26

Marks: 1 (Budgeted Time 1 Min)

A particular half-adder has _____ inputs and _____ output(s).

Answer (Please select your correct option)

3, 1

3, 2

2, 1

2, 2

correct

Made By: Waqar Siddhu

Question No : 16 of 26

Marks: 1 (Budgeted Time 1 Min)

TTL based devices work with a DC supply of ____ Volts

Answer (Please select your correct option)

+10

+5

correct

+3

3.3

Made By: Waqar Siddhu

Question No : 17 of 26

Marks: 1 (Budgeted Time 1 Min)

In CMOS 5 Volt series, Input voltage for Logic high signal (V_{IH}) is in the range of _____ volts.

Answer (Please select your correct option)

3.5 to 5

correct

4.5 to 5

0 to 5

0 to 3.5

Made By: Waqar Siddhu

Question No : 18 of 26

Marks: 1 (Budgeted Time 1 Min)

A multiplexer circuit has _____ input(s) and _____ output(s).

Answer (Please select your correct option)

Single, single

Single, multiple

Multiple, single

Multiple, multiple

correct

Made By: Waqar Siddhu

Question No : 19 of 26

Marks: 1 (Budgeted Time 1 Min)

The binary values for the standard SOP expression, $ABCD + \bar{A}BCD + ABC\bar{D}$ are _____

Answer (Please select your correct option)

1110 + 0110 + 0001

correct

1011 + 1111 + 1011

0001 + 1001 + 1110

1010 + 1110 + 0101

Made By: Waqar Siddhu

Question No : 20 of 26

Marks: 1 (Budgeted Time 1 Min)

Determine the binary values of the variables for the following standard POS expression.
 $(A + B + C)(A + B + \bar{C})$

Answer (Please select your correct option)

(1 + 0 + 1)(0 + 1 + 0)

CORRECT

(0 + 1 + 0)(1 + 0 + 1)

(1 + 0 + 0)(0 + 0 + 1)

(0 + 1 + 0)(1 + 1 + 0)

Made By: Waqar Siddhu

Question No : 21 of 26

Marks: 2 (Budgeted Time 4 Min)

How many possible outputs does a decoder of 3 inputs contain?

Answer (Please click here to Add Answer)



Made By: Waqar Siddhu

Question No : 22 of 26

Marks: 2 (Budgeted Time 4 Min)

How can we use 3-to-8 decoder to implement SOP expressions?

Answer (Please click here to Add Answer)



Made By: Waqar Siddhu

Question No : 23 of 26

Marks: 3 (Budgeted Time 6 Min)

For a two bit comparator circuit, specify all the inputs for which $A > B$ is set to 1.

Answer ([Please click here to Add Answer](#))




Made By: Waqar Siddhu

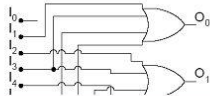
Question No : 24 of 26

Marks: 3 (Budgeted Time 6 Min)

Identify the following circuit that is which combinational circuit is being represented by this diagram?



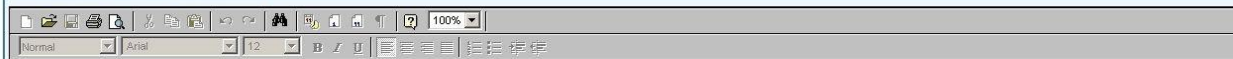
Answer ([Please click here to Add Answer](#))



Made By: Waqar Siddhu

Question No : 24 of 26

Marks: 3 (Budgeted Time 6 Min)

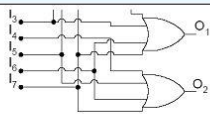

Answer ([Please click here to Add Answer](#))



Made By: Waqar Siddhu

Question No : 25 of 26

Marks: 5 (Budgeted Time 10 Min)

Consider a logical circuit for 4-bit binary number. The circuit gives output 0 for adjacent 0s in a binary number. Draw the karnaugh map of such circuit and derive simplified POS expression.

Answer ([Please click here to Add Answer](#))



Made By: Waqar Siddhu

Question No : 26 of 26

Marks: 5 (Budgeted Time 10 Min)

Multiplexers can be used as a "Logic Function Generator". Draw only circuit diagram and function table based on three variables.

Answer ([Please click here to Add Answer](#))



Made By: Waqar Siddhu